

$$1. a) i_2 = \frac{2V}{R_1 + \frac{R}{2}}$$

Answers Test 2 2009


$$b) i = \frac{2V}{R_1 + R} ; Q = 2VC \frac{R}{R_1 + R}$$

$$2. a) \tilde{Q}_1 - \tilde{Q}_2 = C_1 V_1$$

$$b) \tilde{Q}_2 = (V_2 - V_1) \frac{C_1 C_2}{C_1 + C_2}$$

$$3. a) x < T/2 \quad E_1 = \frac{\rho x}{\epsilon_0}$$
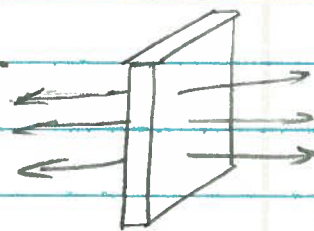
$$x > T/2 \quad E_2 = \frac{\rho T}{2\epsilon_0}$$



$$b) V(L + \frac{T}{2}) - V(0) = -\frac{\rho T^2}{8\epsilon_0} - \frac{\rho T}{2\epsilon_0} L$$

$$4. a) j = \frac{i}{2\pi r W} \text{ radially out}$$

$$b) V(a) - V(b) = \frac{\rho i}{2\pi W} \ln \frac{b}{a}$$

$$c) R = \frac{V}{i} = \frac{\rho}{2\pi W} \ln \frac{b}{a}$$