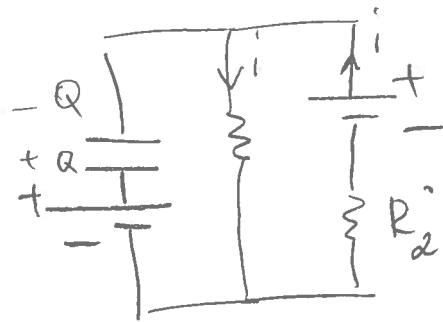


Exam 2 2015


1. $i = \frac{V_2}{R_1 + R_2}$

$$Q = C \left(V_1 - V_2 \frac{R_1}{R_1 + R_2} \right)$$

$$i = 1 \text{ A}; \quad Q = 6 \cdot 10^{-6} \text{ C}$$



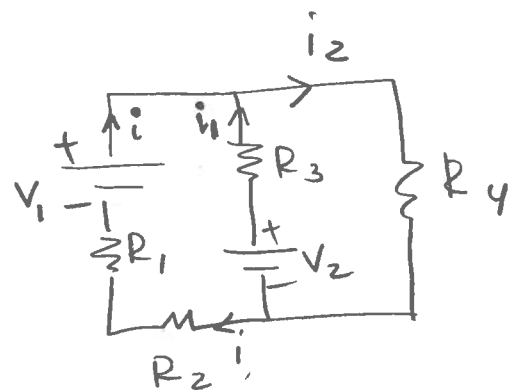2. $i_1 = 1 \text{ A}; \quad i = 1 \text{ A}; \quad i_2 = 2 \text{ A}$



$$3. \quad V(D) - V(O) = - \left[\frac{Q}{4\pi\epsilon_0 L} + \frac{Q}{2\pi\epsilon_0 L} \ln 2 + \frac{Q}{2\pi\epsilon_0 L} \ln 2 \right] =$$

$$= - \left[\frac{Q}{4\pi\epsilon_0 L} + \frac{Q}{\pi L \epsilon_0} \ln 2 \right]$$

4. $i = \frac{2aV}{8_0 L}$

$$Q = \frac{\epsilon_0 a V}{2L}$$