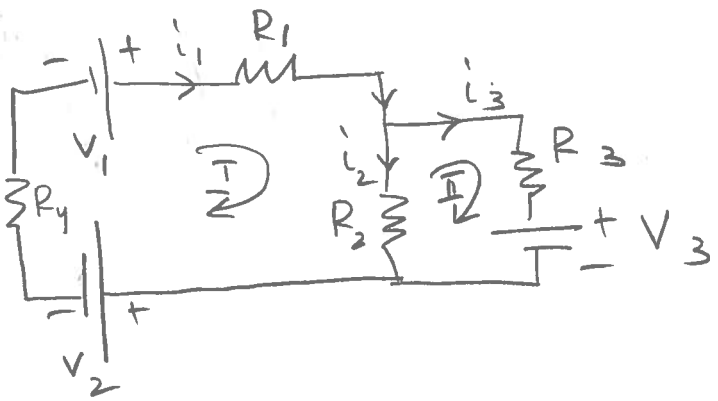


Answers Exam 2 2018

1. $i_1 = i_2 + i_3$

$$-V_1 + i_1 R_1 + i_2 R_2 + V_2 + i_1 R_4 = 0$$


$$i_3 R_3 + V_3 - i_2 R_2 = 0$$



2. a) $i = \frac{V}{R_1 + R_2 + R_3}$

$$Q_1 = C_1 R_2 i$$

$$Q_2 = C_2 R_3 i$$

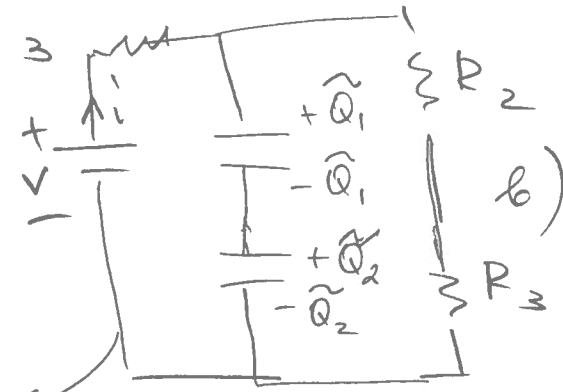

b)

$$\left\{ \begin{array}{l} -V + iR_1 + iR_2 + iR_3 = 0 \\ -V + iR_1 + \frac{\tilde{Q}_1}{C_1} + \frac{\tilde{Q}_2}{C_2} = 0 \\ -Q_1 + Q_2 = -\tilde{Q}_1 + \tilde{Q}_2 \end{array} \right.$$

3. $V(2R_2) - V(0) = -\frac{\rho R_1^2}{4\epsilon_0} - \frac{\rho R_1^2}{2\epsilon_0} \ln 2$

4. $V(b) - V(a) = \frac{\rho_1 i}{4\pi} \left(\frac{1}{R_B} - \frac{1}{R_A} \right) + \frac{\rho_2 i}{4\pi} \left(\frac{1}{R_C} - \frac{1}{R_B} \right)$