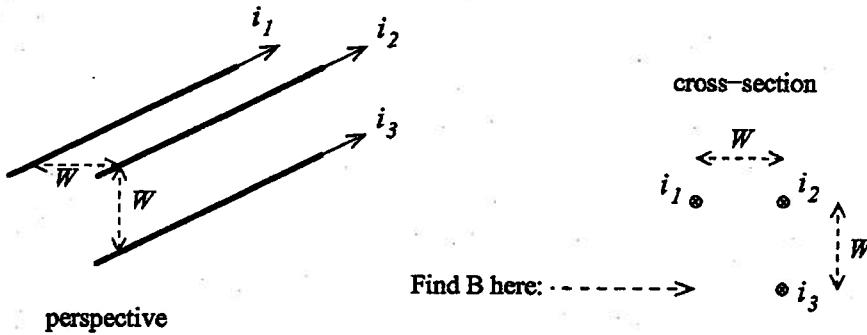


Print your name: _____

Physics 208: Electricity and Magnetism, Exam 3

Problem 1. 25 points.

(a) There are three very long, extremely thin, parallel wires. One with current i_1 and one with i_2 and one with i_3 . In cross-section, the wires are located at the corners of a square of side W . If all currents flow into the page, find the magnetic field vector at the fourth corner.



(b) What would be the force on a length H of wire if it was parallel to the other wires at the fourth corner and had a current i_4 coming out of the page?


Be neat. Neatness helps. Work *neatly*.

Print your name: _____

Physics 208: Electricity and Magnetism, Exam 3

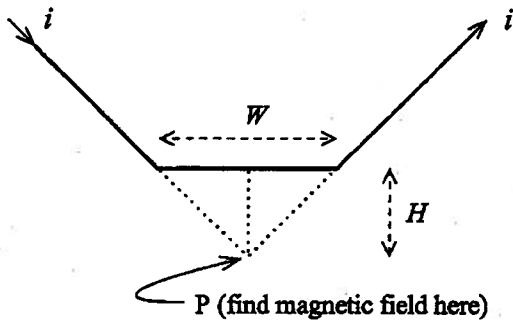Problem 2. 25 points.

A very long thin wire carries a current i . It has the shape and dimensions shown below.



Find the magnetic field at the point P .


If you work neatly I will find more partial credit for you!

Print your name: _____

Physics 208: Electricity and Magnetism, Exam 3

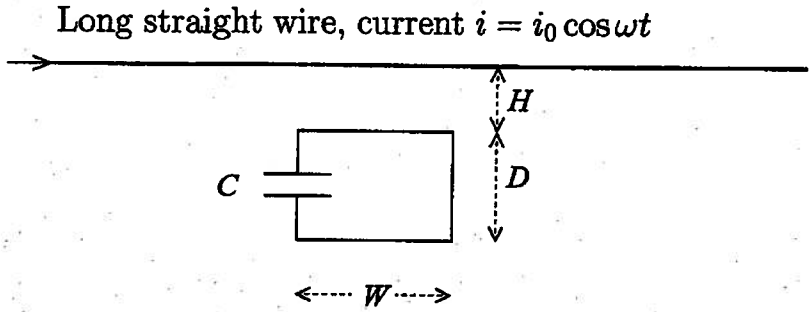Problem 3. 25 points.

A rectangular circuit containing a capacitor C is located near an infinitely long narrow wire carrying a current $i_0 \cos \omega t$ where i_0 and ω are constants. The circuit has no resistance and its self-inductance can be ignored. Find the charge on the top capacitor plate as a function of time.




Make sure you are being neat. Working neatly will help you get it right.

Print your name: _____

Physics 208: Electricity and Magnetism, Exam 3


Problem 4. (25 points)

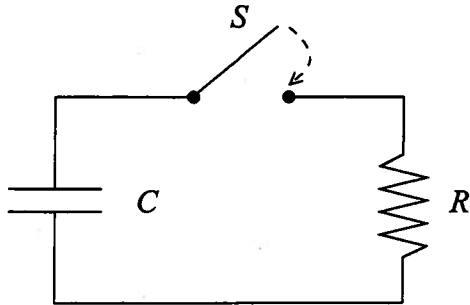(a) In the circuit below, the capacitor is originally charged with Q_0 on the top plate, and $-Q_0$ on the bottom. At $t = 0$ the switch S is closed. Please note that all wires in this circuit have no resistance.



Derive the equation for the charge on the capacitor as a function of time assuming the self-inductance of the circuit can be ignored. Solve the equation.

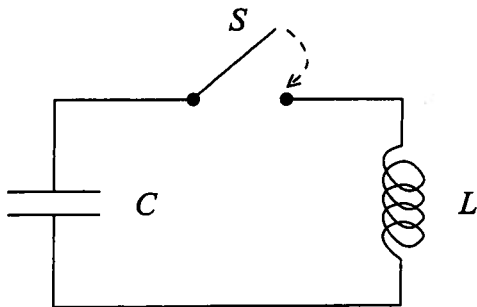(b) In the circuit below, the capacitor is originally charged with Q_0 on the top plate, and $-Q_0$ on the bottom. At $t = 0$ the switch S is closed. Derive the equation for the charge on the plates as a function of time if the self-inductance of the circuit is L and the resistance of the circuit is negligible. Solve the equation.



Work neatly! If you are neat, I can read what you did and maybe find more points for you.