

# EXAM III Physics 208 2011

Name.....Section Number.....

## USEFUL INFORMATION

For two point particles

$$\vec{F} = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} \hat{r}$$

$$d\vec{B} = \frac{\mu_0 i}{4\pi} \frac{d\vec{S} \times \vec{r}}{r^3}$$

$$\frac{d\vec{r}}{dt} = \frac{dx}{dt} \vec{i}_x + \frac{dy}{dt} \vec{i}_y = \frac{dr}{dt} \vec{i}_r + r \frac{d\theta}{dt} \vec{i}_\theta$$

$$\oint \vec{E} \cdot d\vec{r} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{S}$$

$$C = \frac{Q}{V} \quad R = \rho \frac{l}{A}$$

$$\int \vec{B} \cdot d\vec{S} = \pm Li$$

$$\oint \vec{B} \cdot d\vec{r} = \mu_0 i_{\text{enclosed}}$$

1.


2.

3.


4.

---

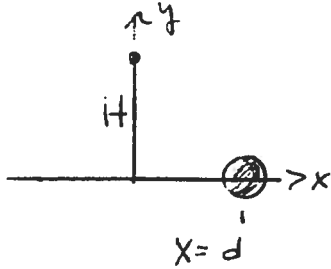
1. (25 points) An infinitely long wire carrying a current  $i$  directed into the page ( $-\vec{i}_z$ ) has a circular cross section of radius  $W$ . The current is uniformly spread over the cross sectional area.
- a. If the center of the wire is on the  $x$  axis at  $x = d$ , find the  $x$  and  $y$  components of the magnetic field at the point with  $x = 0$  and  $y = H$ .



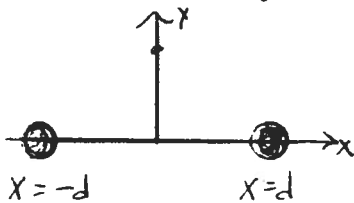
- b. If a second, identical wire, also with current  $i$  into the page, has its center on the  $x$  axis at  $x = -d$ , find the total magnetic field due to both wires at the point at  $y = H$  on the  $y$  axis.



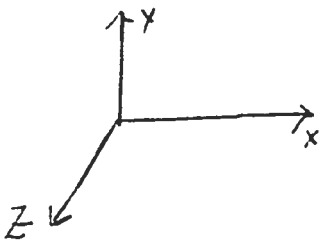
- c. If a particle with positive charge  $q$  had velocity  $\vec{v} = v_0 \vec{i}_z$ , at the point  $x = 0$  and  $y = H$  what would be the magnetic force on it?



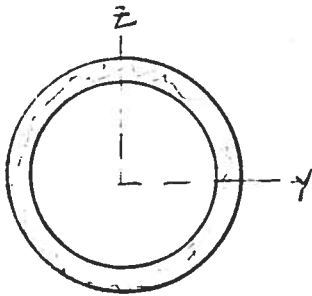
2. (25 points) A circular loop of wire with radius  $H$  is made of wire which has resistivity  $\rho$  and cross sectional area  $a$ . It is in the  $y, z$  plane with its center at the origin.
- a. If a magnetic field given by  $\vec{B} = B_0 \sin \beta t \vec{i}_x$  is present, find the current that will flow in the loop, ignoring the self inductance of the loop. Here  $B_0$  and  $\beta$  are known constants and  $\vec{i}_x$  points out of the page.



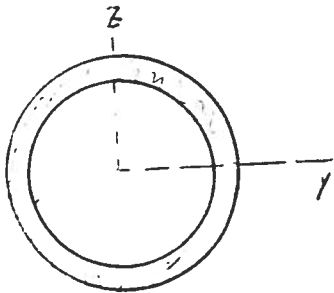- b. Find the current in the loop if instead the magnetic field was  $\vec{B} = B_0(1 - \frac{r}{2H}) \sin \beta t \vec{i}_x$  where  $r$  is the distance from the origin.




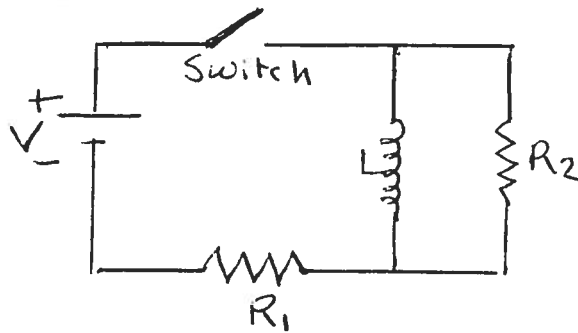3. (25 points) In the circuit below all self inductance is assumed to be contained in the coil which has inductance  $L$ .



- a. If the switch has been closed for a long time so that the steady state has been reached, find the currents in the resistors.
- b. If the switch is now opened, at  $t = 0$ , find the current through the coil as a function of time. Clearly show how you obtain the result.

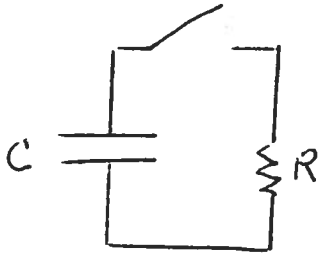4. (25 points) In the circuit below the capacitor is originally charged with  $Q_0$  on the top plate and  $-Q_0$  on the bottom. At  $t = 0$  the switch is closed.
- a. Find the charge on the plates and the current through the resistor as functions of time assuming the self inductance of the circuit can be ignored.



- b. In the circuit below the capacitor  $C_2$  is initially uncharged and  $C_1$  has charge  $Q_0$ . At  $t = 0$  the switch is closed. Find the charges on the capacitors as a function of time assuming the self inductance of the circuit can be ignored.

